

a) $Z_{ie} = ? \quad X_1 = \omega L_1 = 2\pi f \cdot L_1 = 2\pi \cdot 275 \text{ Hz} \cdot 100 \text{ mH} = (172,8 \Omega) \approx 173 \Omega$

$X_2 = \omega L_2 = 2\pi f L_2 = 431,9 \Omega \approx 432 \Omega$

$\Rightarrow Z_1 = 10 \Omega + j 173 \Omega$

$\Rightarrow Z_2 = 25 \Omega + j 432 \Omega$

$$Z_{ie} = \left(\left(\left(R_{1, \text{gen}} \oplus R_1 \right) \parallel R_2 \right) \oplus Z_1 \right) \parallel R_3 \oplus Z_2 = \left(Z_1 \parallel R_3 \right) \oplus Z_2 \approx 155 \Omega + j 580 \Omega$$

$\frac{50 \Omega + 330 \Omega = 380 \Omega}{380 \Omega \parallel 220 \Omega = 138 \frac{1}{3} \Omega}$
 $\frac{10 \Omega + 330 \Omega = 340 \Omega}{340 \Omega \parallel 220 \Omega = 138 \frac{1}{3} \Omega}$
 $\frac{138 \frac{1}{3} \Omega + 10 \Omega + j 173 \Omega = 148 \frac{1}{3} \Omega + j 173 \Omega}{= Z_1}$
 $\frac{129,9 \Omega + 147,5 \Omega \approx 277,4 \Omega}{\approx 155 \Omega + j 580 \Omega}$

$\Rightarrow R_{ie} = 155 \Omega$

$\Rightarrow X_{ie} = 580 \Omega$

$|Z_{ie}| = \sqrt{R_{ie}^2 + X_{ie}^2} = \sqrt{(155 \Omega)^2 + (580 \Omega)^2} \approx 600 \Omega$

b) $R_a = |Z_{ie}| = 600 \Omega$

$P_a = \frac{U_a^2}{2(R_i + R_a)} = \frac{(2V)^2}{2(155 \Omega + 600 \Omega)} = 2,65 \text{ mW}$

c) $P_{a, \text{max}} = \frac{U_a^2}{4R_i} = \frac{4V^2}{4 \cdot (155 \Omega)} = 6,45 \text{ mW}$

d) $R_{ie} = \left(\left(\frac{U_L}{U_a} \right)^2 R_a^2 - R_a^2 - \left(\frac{U_L}{I_k} \right)^2 \right) \cdot \frac{1}{2 \cdot R_a}$

①

$U_{L, \text{mV}}$	622
$I_{k, \text{mA}}$	1,06

$R_a = 500 \Omega \Rightarrow U_a = 356 \text{ mV}$

$R_{ie} = \left[\left(\frac{U_L}{U_a} \right)^2 R_a^2 - R_a^2 - \left(\frac{U_L}{I_k} \right)^2 \right] \cdot \frac{1}{2 R_a} = \left[\left(\frac{622 \text{ mV}}{356 \text{ mV}} \right)^2 \cdot 500 \Omega^2 - 500 \Omega^2 - \left(\frac{622 \text{ mV}}{1,06 \text{ mA}} \right)^2 \right] \cdot \frac{1}{2 \cdot 500 \Omega}$

$R_{ie} = 187 \Omega \checkmark$

$Z_{ie} = \frac{U_L}{I_k} = \frac{622 \text{ mV}}{1,06 \text{ mA}} = 586 \Omega \checkmark$

$\Rightarrow X_{ie} = \sqrt{Z_{ie}^2 - R_{ie}^2} = \sqrt{(586 \Omega)^2 - (187 \Omega)^2} = 555 \Omega$

$X_{ie} = 555 \Omega \checkmark$

Gemessene Werte werden aufgrund der Bauteiltoleranzen und Messungenauigkeit ab!

R_a/Ω	100	200	300	400	450	500	550	600	700	800	900
U/mV	89	187	254	312	337	358	377	395	424	447	467
$P/\mu W$	79	174	215	243	<u>252</u>	256	258	<u>260</u>	257	249	242
R_a/Ω	1000										
U/mV	483										
$P/\mu W$	233										

↑
Betragsgangmessung
✓

$$P = \frac{U^2}{R_a} = \frac{(89 \text{ mV})^2}{100} = \underline{\underline{79 \mu W}}$$

$$P_{\max} (R_a = 600 \Omega) = \underline{\underline{260 \mu W}}$$

R_a/Ω	100	200	300	400	450	500	550	600	700	800	900
U/mV	172	227	305	360	383	402	420	434	459	479	495
$P/\mu W$	148	257	310	324	<u>326</u>	323	321	314	301	287	272
R_a/Ω	1000										
U/mV	508										
$P/\mu W$	258										

$$P_{\max} (R_a = 450 \Omega) = \underline{\underline{326 \mu W}}$$

$\textcircled{4}$ R_a/Ω	100	200	300	400	450	500	550	600	700	800	900
U/mV	240	334	397	438	453	466	478	488	504	517	527
$P/\mu\text{W}$	576	<u>578</u>	525	479	456	434	415	396	362	334	308
R_a/Ω	1000	↑ Leistungsanpassung ✓									
U/mV	536										
$P/\mu\text{W}$	287										

$$P_{\text{max}}(R_a = 200\Omega) = \underline{\underline{578\mu\text{W}}}$$

$$R_{\text{opt}} = 187\Omega$$

R_{opt}	187 Ω
U_1	328 mV
I_a	3,12 mA
P_{opt}	<u>575μW</u>

~~$$P_{\text{opt}} = U_1 \cdot I_a$$~~

