

I.3.5

$$\frac{U_2}{U_1} = \frac{1}{10} = \frac{R_e}{R_T + R_e} \Rightarrow \frac{R_T + R_e}{10} = R_e$$

$$R_T = 10 \cdot R_e - R_e \\ = 90 \cdot 10^6 \Omega$$

$$a) \frac{U_2}{U_1} = \frac{R_e \parallel R_c}{R_T + (R_e \parallel R_c)} = \frac{R_e}{p \cdot C_e \cdot R_e \cdot R_T + R_e + R_T}$$

$$H(p) = \frac{R_e}{C_e \cdot R_e \cdot R_T} \cdot \frac{1}{p + \frac{R_c + R_T}{C_e \cdot R_e \cdot R_T}} \quad p + \frac{R_c + R_T}{C_e \cdot R_e \cdot R_T} = 0$$

$$f_g = \frac{R_c + R_T}{2\pi C_e R_e R_T} = 824,19 \text{ Hz}$$

$$b) \frac{U_2}{U_1} = \frac{R_e \parallel C_e \cdot p}{R_T \parallel C_T \cdot p + R_e \parallel C_e \cdot p} = \frac{R_e \cdot C_T \cdot R_T \cdot (p + \frac{1}{R_T \cdot C_T})}{R_e \cdot R_T \cdot (C_e + C_T) \cdot (p + \frac{R_e + R_T}{R_e \cdot R_T (C_e + C_T)})}$$


$$\sigma_{01} = p + \frac{1}{R_T \cdot C_T} = 0$$

$$f_{01} = \frac{1}{2\pi R_T C_T}$$

$$\sigma_1 = p + \frac{R_e + R_T}{R_e R_T (C_e + C_T)} = 0$$

$$f_1 = \frac{R_e + R_T}{R_e R_T (C_e + C_T) \cdot 2\pi}$$

Pol nicht nach rechts
Null " " links


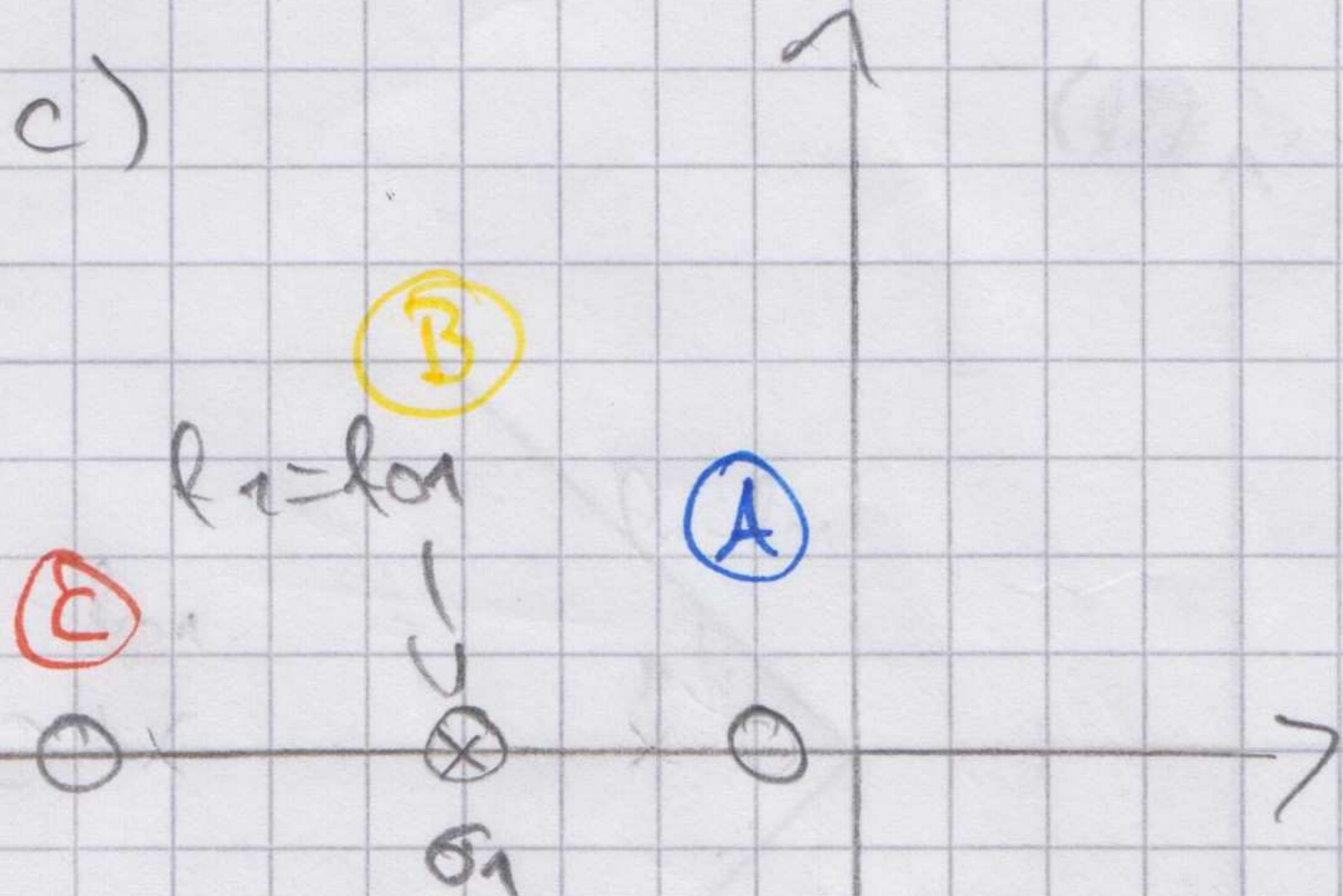


(Diagram auf Rückseite!)

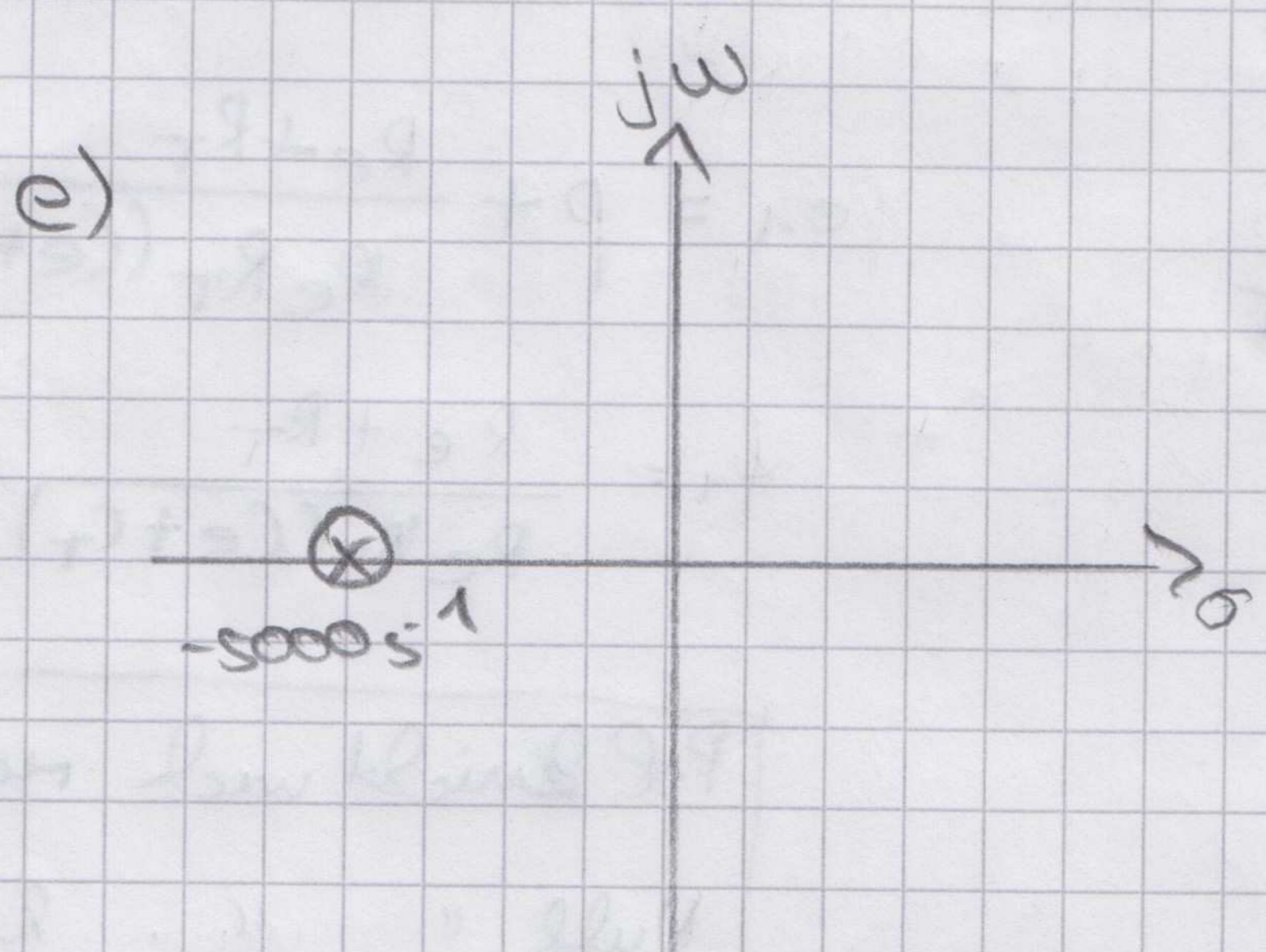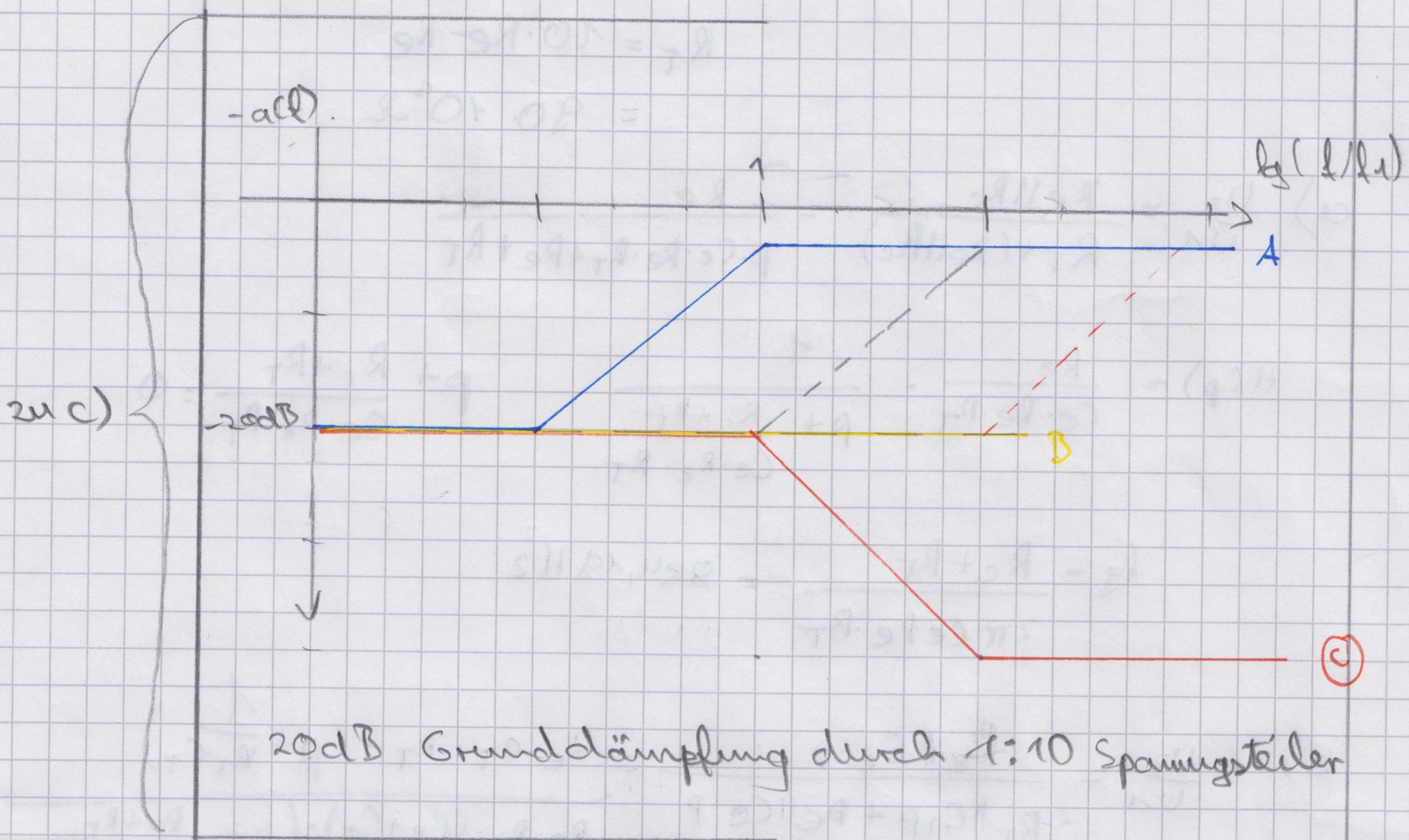f) $f_{3dB} = \infty$

→ wenn f_{3dB} nicht vorhanden, dann immer ∞ ?

$$d) \frac{1}{R_T \cdot C_T \cdot 2\pi} = \frac{R_e + R_T}{R_e \cdot R_T \cdot (C_e + C_T) \cdot 2\pi} \Rightarrow C_T = \frac{C_e \cdot R_e}{R_T} = 2,222 \cdot 10^{-12} \text{ F}$$



$$f_{01} = f_n = \frac{1}{2\pi R_T C_T}$$

$$\sigma_{01} = \sigma_1 = 2\pi f_1 = -5000 \text{ s}^{-1}$$

